

CSCE 611: Designing a Pipelined MIPS Processor Core



Instructor: Jason D. Bakos



CPU Project


- Goal: design a pipelined processor that can execute 34 MIPS instructions on:

http://www.cse.sc.edu/~jbakos/611/mips/isa_detail.shtml

- Use on-chip memory for program
 - Word addressed
- Use on-chip memory for data
 - Word addressed but with byte-enables
- Recall five steps:
 - fetch, decode, execute, memory, wb




CPU Module (Includes all Stages)

 


Top-Level Design

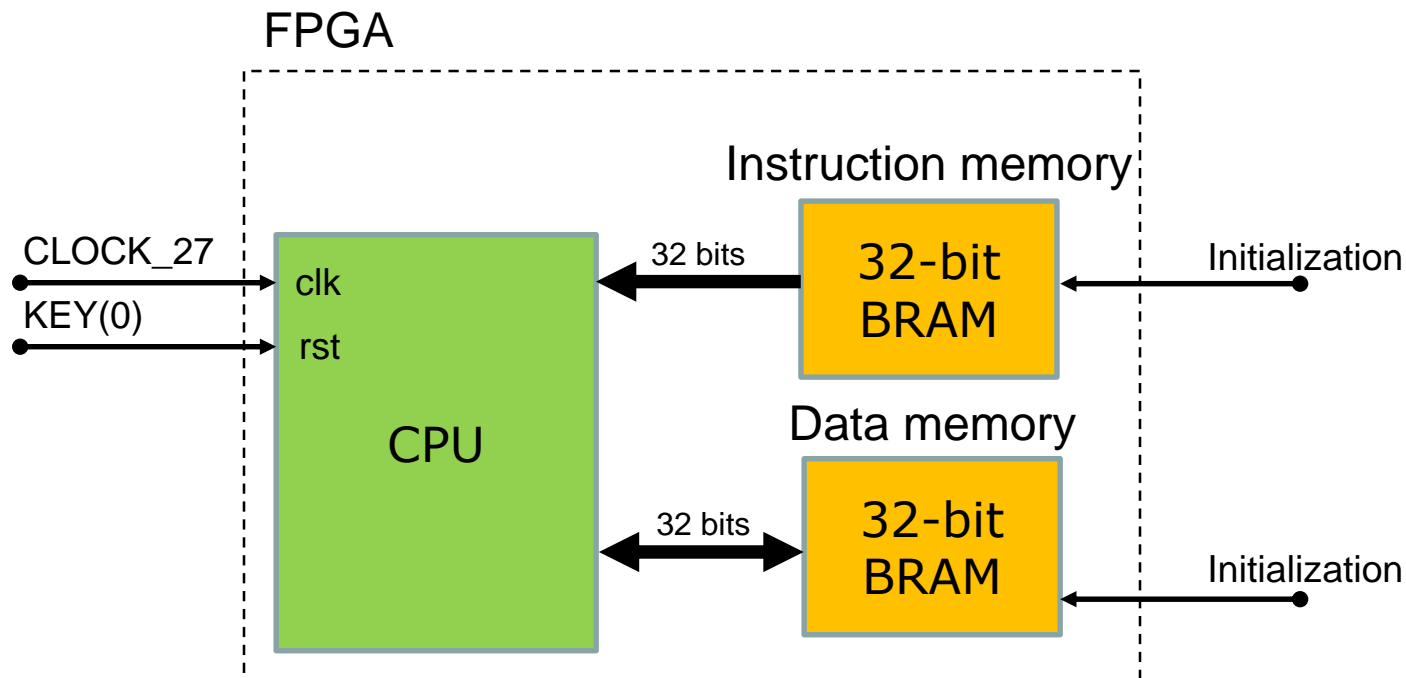- Need two separate memories for instructions and data



Top-Level Design

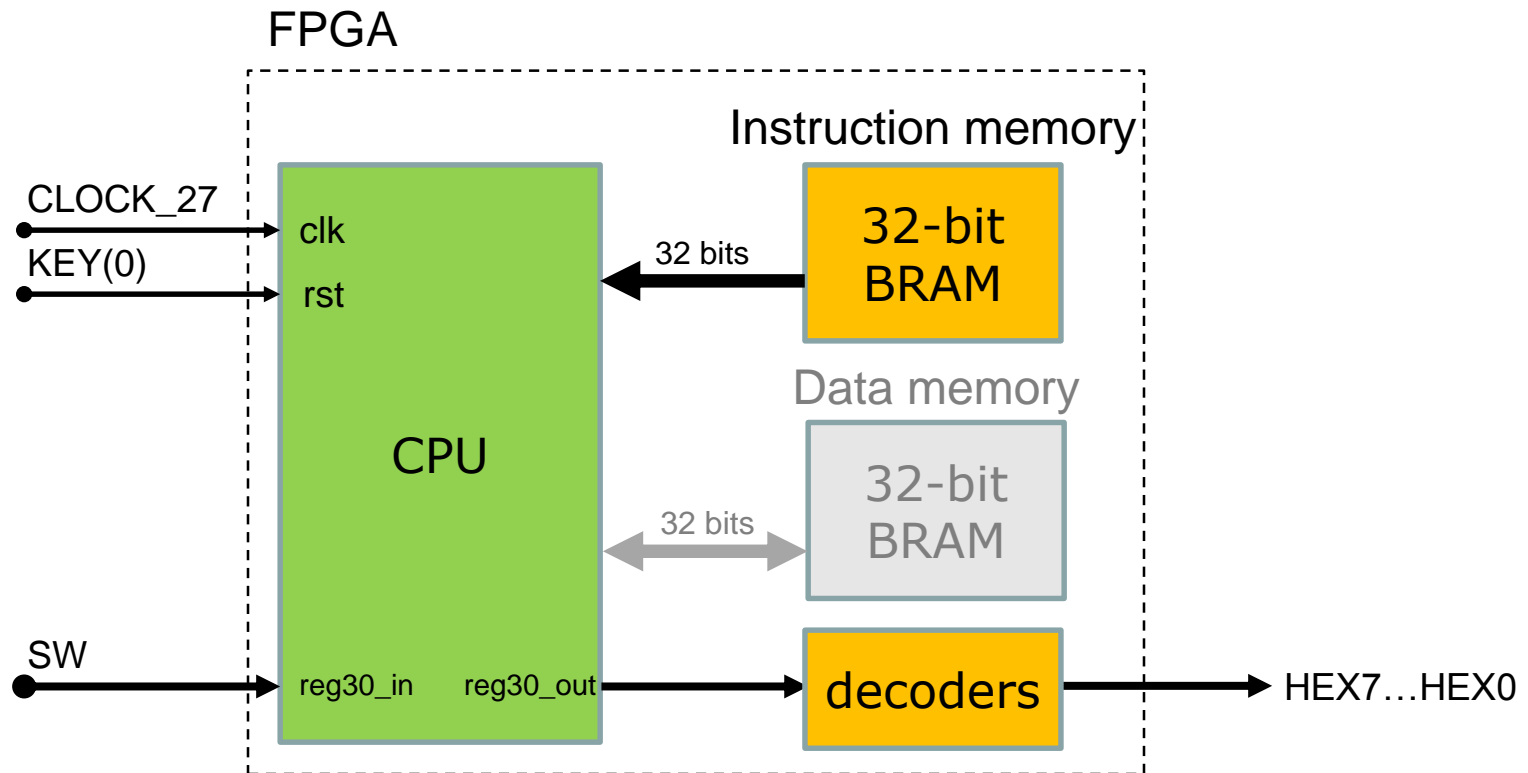- Need two separate memories for instructions and data
 - Each has different characteristics




Execution Stages

- Basic steps: fetch, decode, execute, memory, write back
 - R-type computational instructions (ex. ADD \$1, \$2, \$3):
 - fetch, decode, execute, write back
 - Branch instructions
 - fetch, decode, execute
 - Load instruction
 - fetch, decode, execute, memory, write back
 - Store instruction
 - fetch, decode, memory




Execution Stages

- Single cycle CPU:

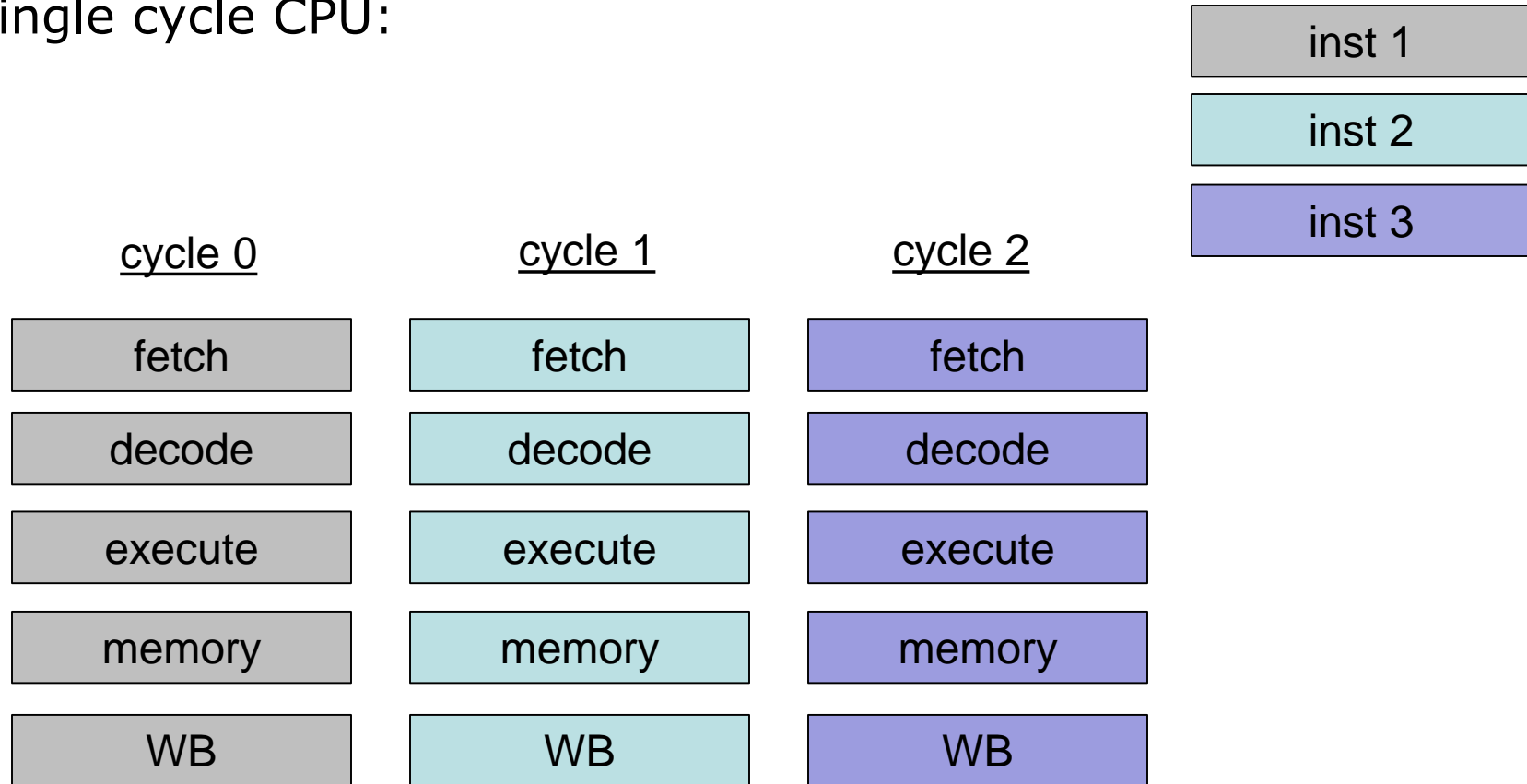


Synchronous Reads

- On-chip memory with synchronous reads

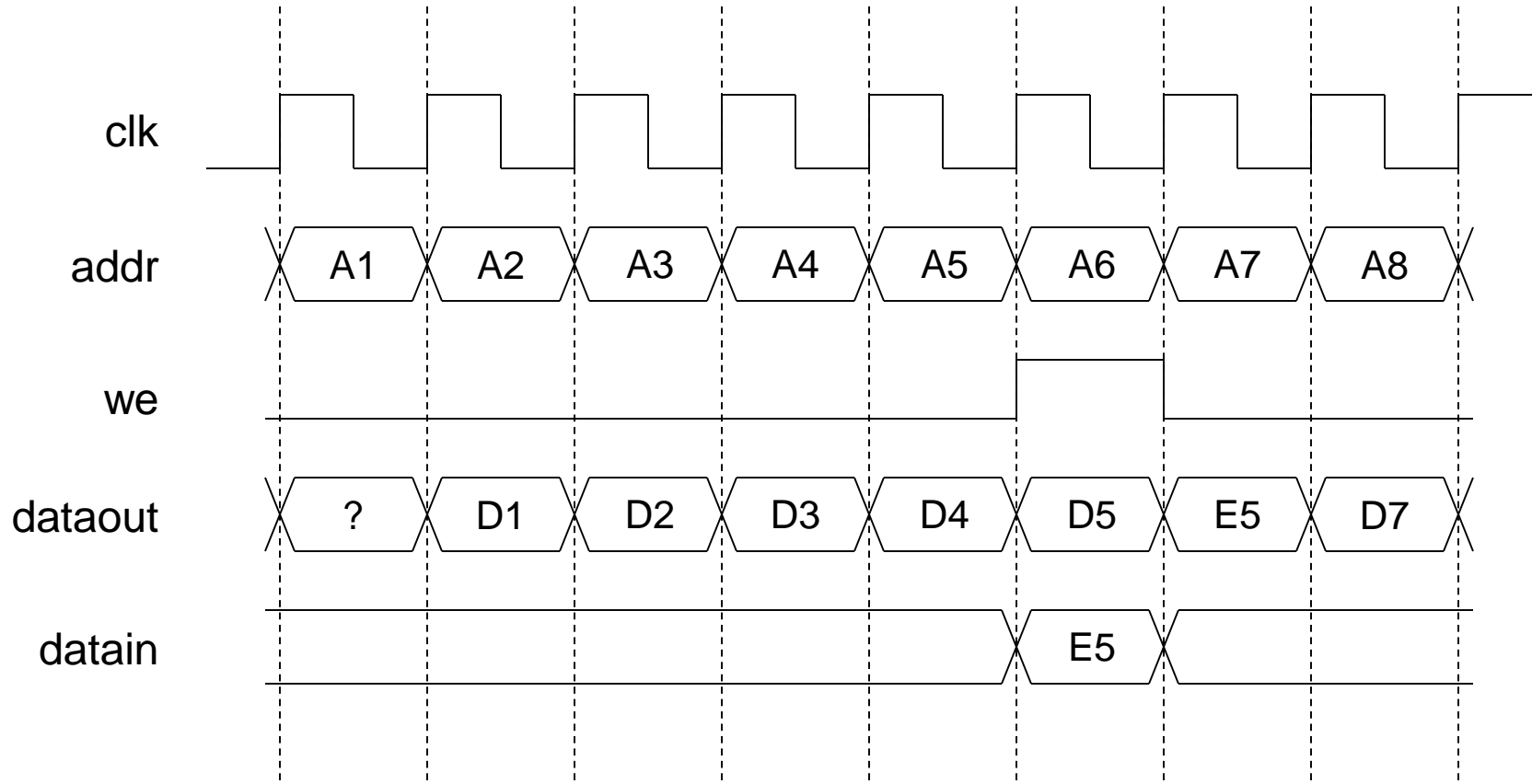


Execution Stages

 

Execution Stages

- Three stage pipeline

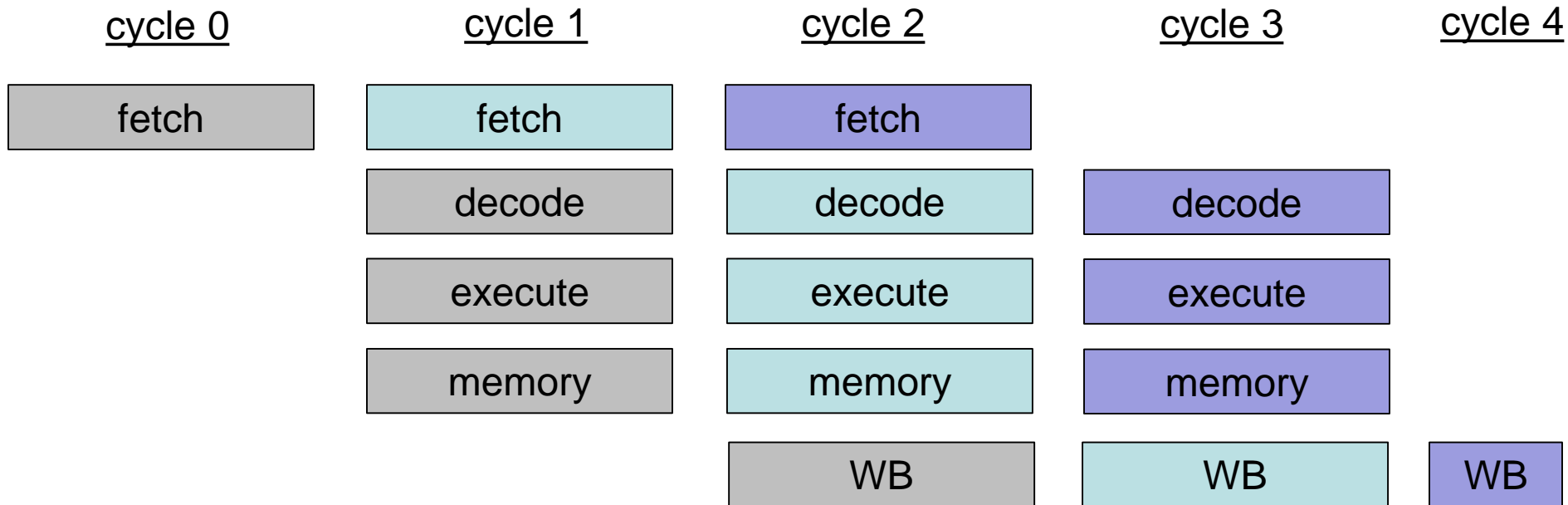

CPU Design

- Loads have a one-cycle latency
 - Need to separate MEM and WB
- Fetches have a one-cycle latency
 - Need to separate FETCH and DECODE
- Solution:
 - Three-stage pipeline:
 - FETCH, DECODE/EX/MEM, WB
 - F E W
 - Add pipeline registers between E and W
 - Loaded data is already delayed, so don't need a register for this
 - Leads to control hazard
 - Must flush FETCH for taken branches
 - Zero-out control signals in if branch is taken in previous cycle


Design Objectives

- Over the next four labs we will design a complete, single-issue pipelined MIPS processor core
 - **Lab 4:** Execute and WB stage supporting all R-type instructions except for JR and JALR
 - Test with a MIPS program that converts binary (switches) to decimal (HEX)
 - **Lab 5:** Support for load and store instructions
 - Test with a MIPS program that performs vector addition and summation
 - **Lab 6:** Support for branch and jump instructions
 - Test with a MIPS program that performs square root




MIPS Fetch Stage

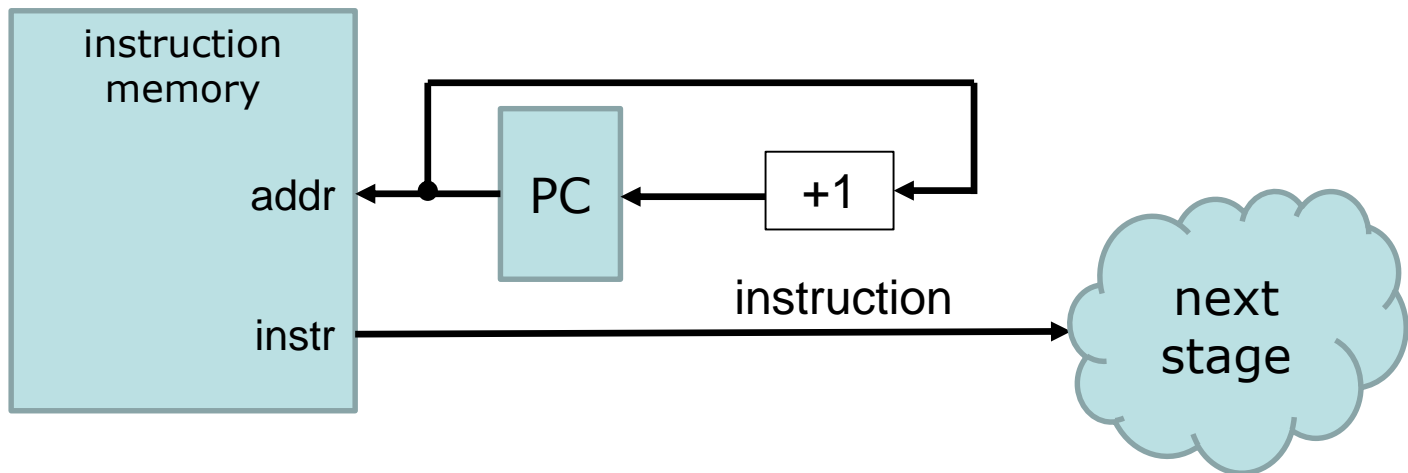- Basic functionality with synchronous instruction memory



Initializing Instruction Memory


- Use script:
 - Use MARS to assemble (F3)
 - File | Dump Memory

 

- Use this file to initialize instruction RAM:

```
initial begin
    $readmemh("hexcode.txt", mem, 0, 1023);
end
```


EX Stage for R-type

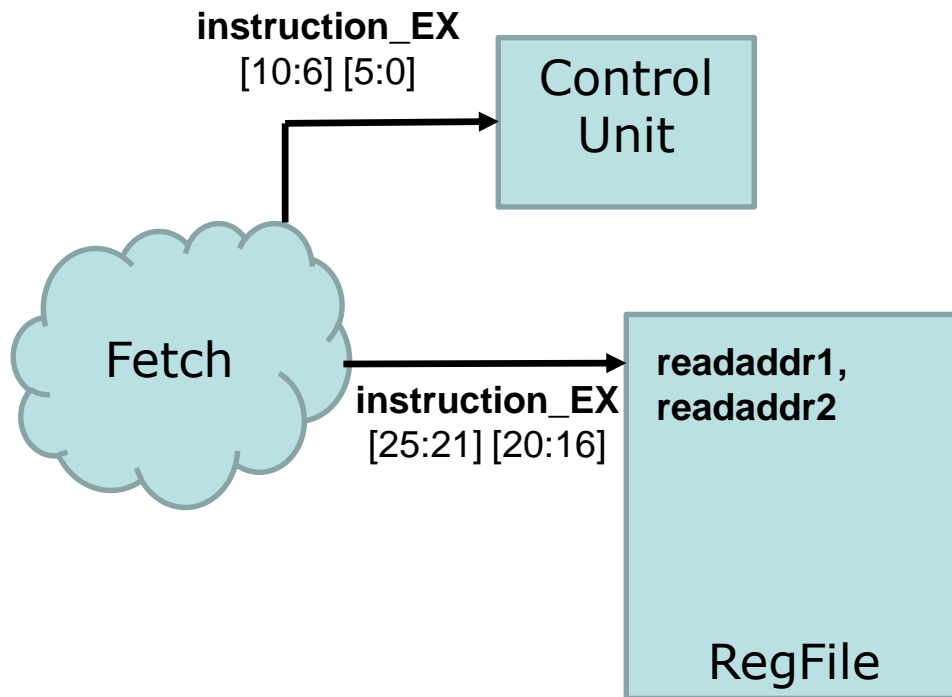


- Objective: fully implement instructions:
 - add, sub, addu, subu, and, or, nor, xor, slt, sltu
 - sll, srl, sra
 - **mult, multu**
 - **mfhi, mflo**
 - **nop**
- Instruction bits:
 - To control unit:
 - [31:26] opcode
 - [10:6] shamt
 - [5:0] function code
 - To register file:
 - [25:21] rs address (to readaddr1)
 - [20:16] rt address (to readaddr2)



EX Stage for R-type

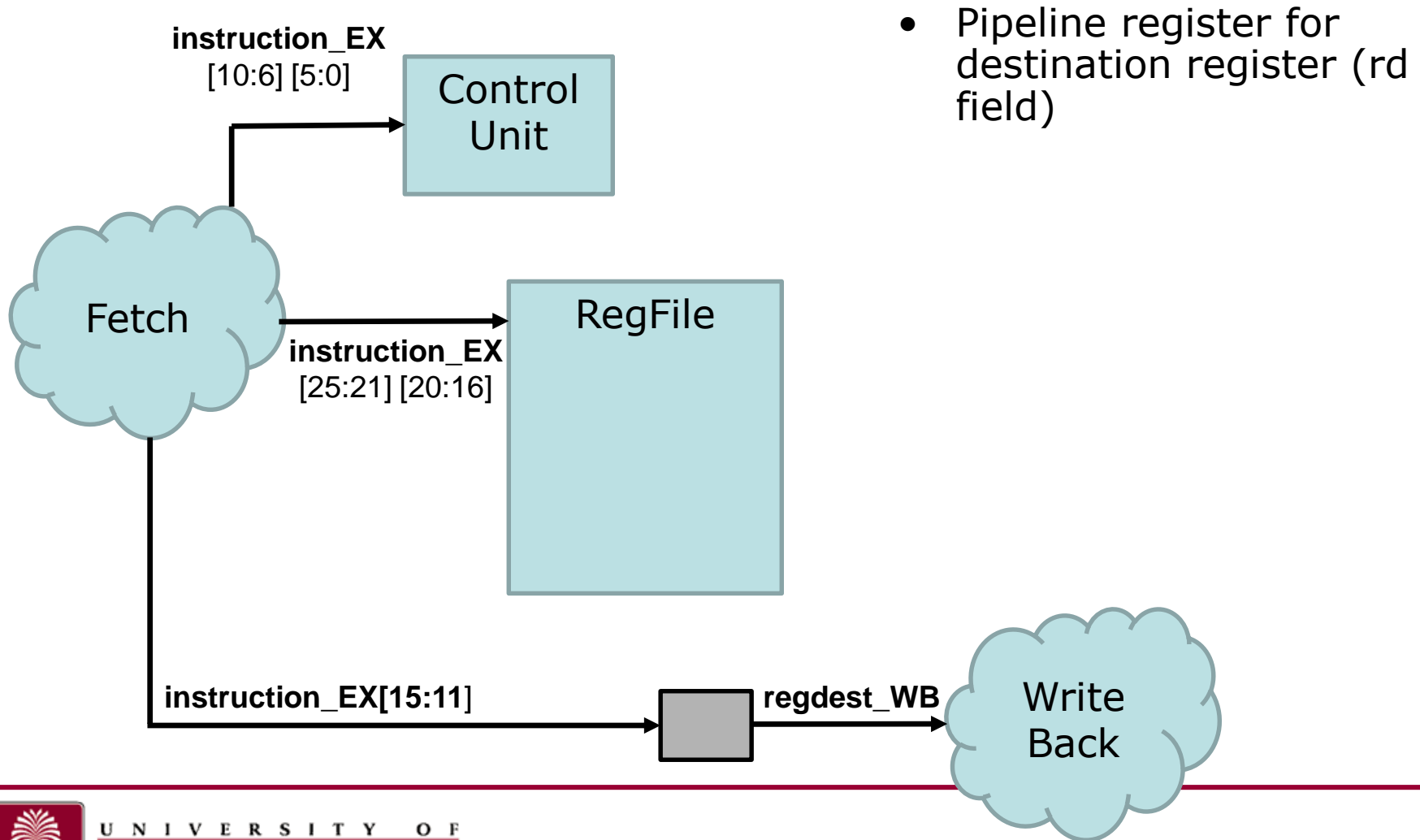


EX Stage for R-type (Additional Signals)

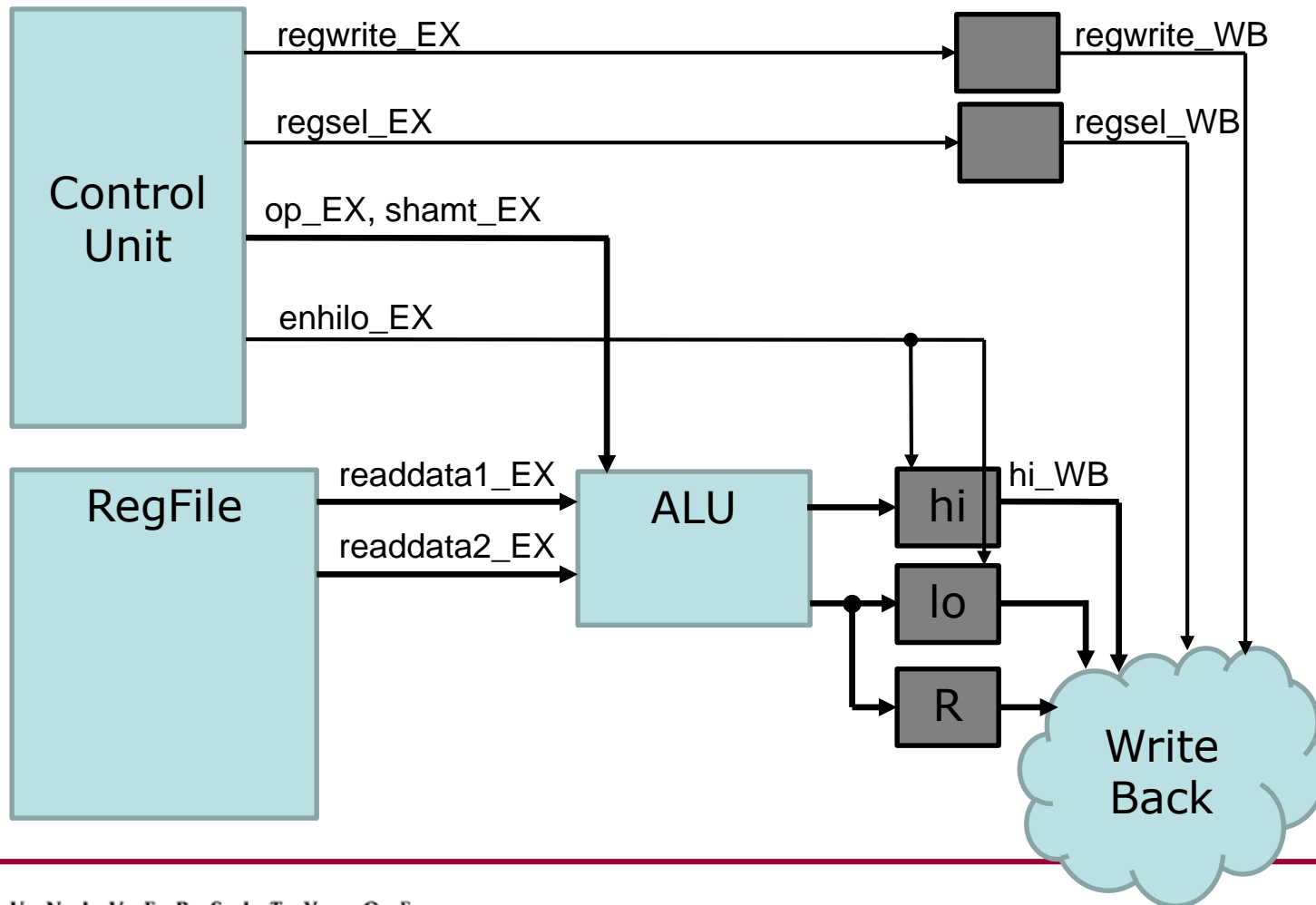

WB Stage for R-type (Extra Signals)

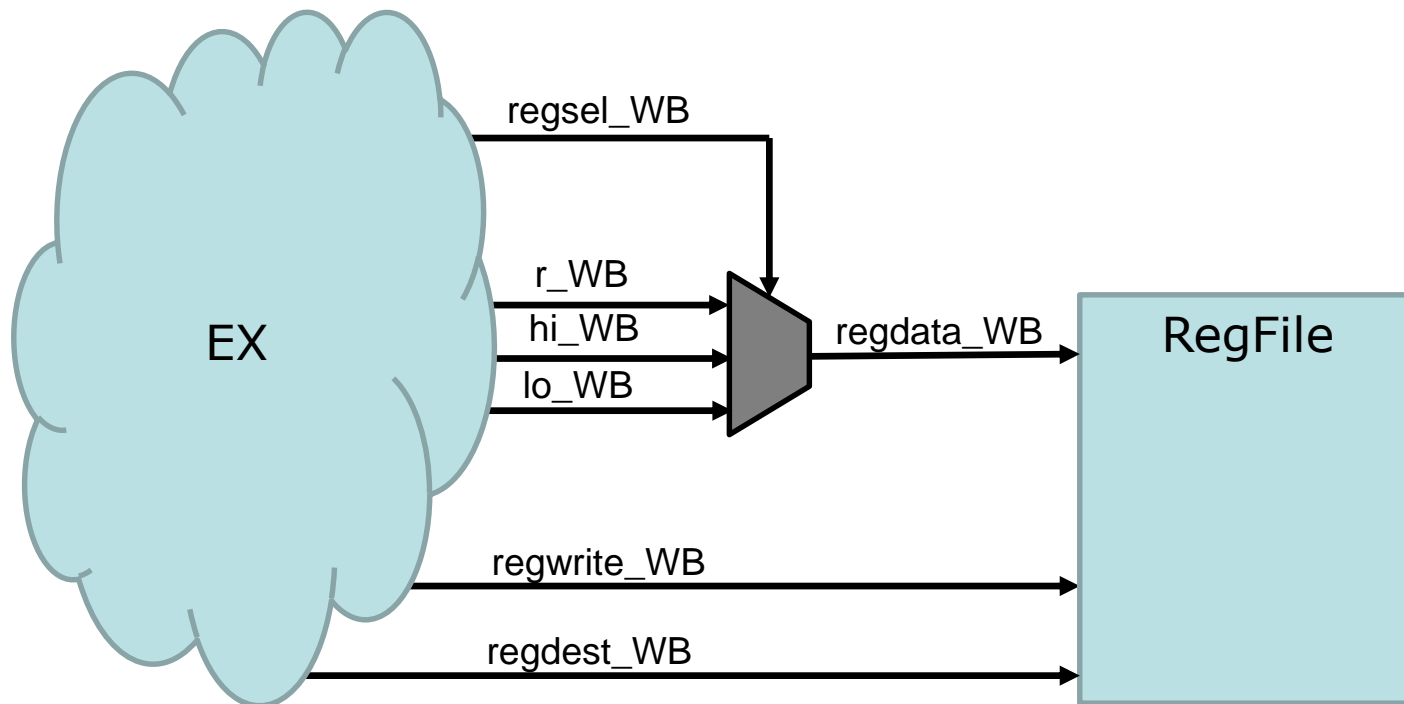- Basically just the write port on the register file



Control Unit for R-type

- Inputs (actual, in CPU design):
 - **instruction_EX[10:6]:** shift amount (used for sll, srl, sra instructions only)
 - **instruction_EX[5:0]:** function code (used for all R-type instructions)
- Outputs:
 - **op_EX[3:0]:** ALU operation (can use don't care X value for mflo, mfhi. nop)
 - **shamt_EX[4:0]:** set to instruction_EX[10:6] for sll, srl, sra, X for everything else
 - **enhilo_EX:** assert for mult/multu instructions
 - **regsel_EX[1:0]:** signal to the WB stage to indicate an ALU write on HI/LO write (1 for mfhi, 2 for mflo, 0 for everything else)
 - **regwrite_EX:** signal to the WB stage to write register (1 for all except MULT/MULTU)

Control Unit Implementation

```
module control_unit (input [5:0] function_code,...);

always @(*) begin
  if ((function_code == 6'b100000) | (function_code == 6'b100001)) begin // add, addu
    alu_op = 4'b0100;
    alu_shamt = 5'bX;
    enhilo = 1'b0;
    regsel = 2'b00;
    regwrite = 1'b1;
  end else if ((function_code == 6'b100010) | (function_code == 6'b100011)) begin // sub, subu
    alu_op = 4'b0101;
    alu_shamt = 5'bX;
    enhilo = 1'b0;
    regsel = 2'b00;
    regwrite = 1'b1;
  ...
  end else if (function_code == 6'b011000) begin // mult (not multu)
    alu_op = 4'b0110;
    alu_shamt = 5'bX;
    enhilo = 1'b1;
    regsel = 2'b00;
    regwrite = 1'b0; ...
  end
```



Example Test Program

```
.text
add $3, $1, $0          # ($3) <= 11
addu $4, $2, $0         # ($4) <= 17
sub $5, $0, $3          # ($5) <= -11
subu $6, $0, $4         # ($6) <= -17
mult $4, $6              # {hi,lo} <= -289
mflo $7                 # ($7) <= -289
mfhi $8                 # ($8) <= -1
multu $4, $6             # {hi,lo} <= 17 * 0xFFFFFFFF
mflo $9                 # ($9) <= -289
mfhi $10                # ($10) <= 16
and $11,$3,$4           # ($11) <= 1
or $12,$3,$4            # ($12) <= 27
xor $13,$3,$4           # ($13) <= 0x0000001A
nor $14,$3,$4           # ($14) <= 0xFFFFFEE4
nop                     # do nothing
sll $15,$3,1            # ($15) <= 22
srl $17,$5,1            # ($17) <= 0x7FFFFFFFA
sra $19,$5,1            # ($19) <= -6
slt $21,$6,$4           # ($21) <= 1
sltu $22,$6,$4          # ($22) <= 0
```



Lab 4: R-type Instructions

- Objectives (due 10/27):
 1. Implement MIPS processor that implements instructions:
`add, sub, addu, subu, mult, multu, and, or, nor, xor, sll, srl, sra, slt, sltu, mfhi, mflo, nop`
 2. Write two test programs:
 - `test_program1.asm`:
 - Tests all instructions (from previous slide)
 - Verify by viewing contents of register file in Modelsim
 - `test_program2.asm`:
 - Read switches as binary value ($0 - 2^{18}-1$)
 - Convert binary from switches to BCD on LEDs
 - Implement on DE2

Binary to Decimal Conversion

val	%10	/10
5678	8	567
567	7	56
56	6	5
5	5	0
0		

- `reg=0`
- `while val != 0`
 - `reg = reg << 4`
 - `reg = reg | val % 10`
 - `val = val / 10`
- This will generate the digits in reverse, so you can connect the least significant BCD digit of the register to the most significant HEX

Work Around Divide

- Our CPU doesn't have a divide or a modulo instruction
- Since we're using a constant factor 10, we can use multiply
- Idea: use fixed-point multiply
 - Assume a decimal point at some location in a value:
 - Example (6,4)-fixed format:

1	0.	1	1	0	1
---	----	---	---	---	---
- $= 2 + 13/16 = 2.8125$
- Now assume we multiply a (32,0) value by a (32,32) value
- Result would be (64,32) value
- Use this to multiply a (32,0) value by 0.1
- (32,32) representation of 0.1 = $2^{32} / 10$



Example

- Assume value = 234
 - Step 1: $\text{temp} = 234 \times 0.1 = 23.4$
 - Step 2: $\text{temp2} = \text{fractional}(\text{temp}) = .4$
 - Step 3: $\text{temp} = \text{whole}(\text{temp}) = 23$
 - Step 4: $\text{digit} = \text{temp2} \times 10 = 4$
 - Step 5: $\text{temp} = \text{temp} \times 0.1 = 2.3$
 - Step 6: $\text{temp2} = \text{fractional}(\text{temp}) = .3$
 - Step 7: $\text{temp} = \text{whole}(\text{temp}) = 2$
 - Step 8: $\text{digit} = \text{temp2} \times 10 = 3$
 - Step 9: $\text{temp} = \text{temp} \times 0.1 = 0.2$
 - Step 10: $\text{temp2} = \text{fractional}(\text{temp}) = .2$
 - Step 11: $\text{temp} = \text{whole}(\text{temp}) = 0$
 - Step 12: $\text{digit} = \text{temp2} \times 10 = 2$
 - Step 13: $\text{temp} == 0$ so finish



Example

- Fixed-point algorithm to convert base-2 integer (32,0) to base-10:
 - $pt_one = 2^{32}/10 = 429496730$
 - $val \leq \text{value to convert}$
 - while $val > 0$
 - $[hi, lo] = val * pt_one$
 - $val = hi$ // val is now $\text{floor}(val/10)$
 - $[hi, lo] = lo * 10$ // hi is now $val \% 10$
 - $digit = hi$ // hi is now floor base-10 LSD
- This algorithm generates the digits from LSD to MSD

Wrapper Design

- For testing on DE2:

```
module de2 (input CLOCK_50, input [3:0] KEY,
            output [6:0] HEX0, ..., output [6:0] HEX7, input [17:0] SW);
// connect DE2 I/Os to CPU/mem/decoders
system my_system (.clk(CLOCK_50), .rst(~KEY[0]),
                  .HEX0(HEX0), ..., .HEX7(HEX7), .SW(SW));
```

- For testing with testbench:

```
module testbench ();
reg clk_tb;
reg rst_tb;
wire [6:0] HEX0;

...

initial begin rst_tb=1; #4; rst_tb=0; end
always begin clk_tb=0; #5; clk_tb=1; #5; end
system my_system (.clk(clk_tb), .rst(rst_tb),
                  .HEX0(HEX0), ..., .HEX7(HEX7), .SW(18'd15));
```



Register Initialization

- In register file, add:

```
initial begin
```

```
    reg[1] <= 32'd <value for 10>
```

```
    reg[2] <= 32'd <value for 0.1>
```

```
end
```